



SCHOOL OF THE WEST

# Electronics

## Chapter 3: Basic Circuit Practise

# **How to build a circuit**

# 4 steps rule

- **Check** that you have the components with the values you need.
- **Design** your circuit on a piece of paper and calculate all the values you need.
- **Simulate** your circuit with some software to check that everything works as expected.
- **Build** your circuit and test it.

# Word of caution



- Electricity can be dangerous. In this course we are dealing with very small voltages and currents, but always pay attention with what you are doing and do not experiment without a previous simulation.
- Do not touch the two terminals of the battery at the same time, or you will become part of the circuit.
- If you go over the maximum power of a component, it will break, burn or even explode, so be careful with your calculations.

# **Our First Circuit**

# Description of the problem


- We have a battery and a lightbulb.
- We want to connect the components to form a circuit so that the light bulb emits light, without burning it.

# Check

- The first step is to check the voltage of our battery. The voltage will be written on it. In our example, it's 9 V.
- Then, for the light bulb, we need to know it's voltage. In our example, we see written on it that it is 9 V.
- A light bulb voltage slightly higher than the battery voltage will also work (it will emit less light), but a lower light bulb voltage will result in the light bulb burning.

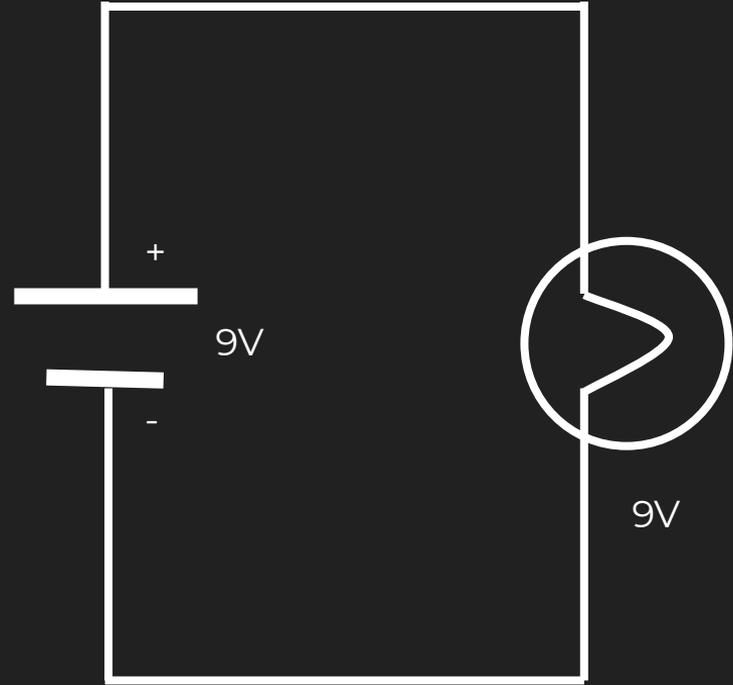
# Design

- Draw a schema with the correct symbols.
- Add the relevant values, in our case the voltage.
- Do all calculations needed. In this example, no calculations are needed.


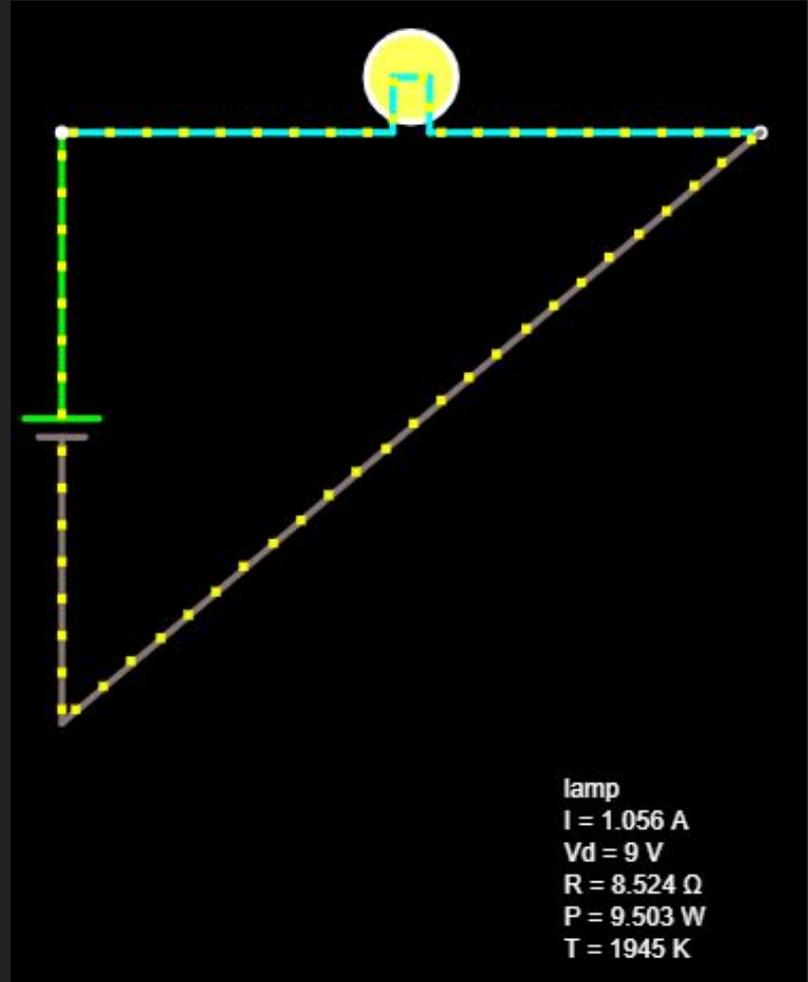
# Simulate

- You can use any simulation software you want. Our recommendation is <http://www.falstad.com/circuit/circuitjs.html?lang=en>
- Recreate your schema in the program and check that all components have the expected voltage value



# Build

- There are many ways to build a circuit. Our suggestion is to use a piece of cardboard as a base.
- As a first step, we will draw the circuit on the cardboard. We will place the components on it and use wire to unite them.
- You will need a tool to cut wires, remove the insulator from their ends. It is usually done with pliers, but scissors can work too.
- In our case, since we want to reuse the components, we will unite wires with electrical tape instead of welding. Make sure the wires make full contact before taping them together



SCHOOL OF THE WEST

**Next lesson**

**Chapter 4: Ohm's law**