



SCHOOL OF THE WEST

Electronics

Chapter 7: Kirchhoff's laws

Maths Review

Systems of equations

- When you have more than one equation related to each other, you have a system of equations.
- There are many ways to solve it: **substitution**, elimination, graphing, matrix solution (Gauss method)...
- We need at least as many equations as we have variables.

For example:

$$2x + 3y - 8z + 85 = 0$$


$$8x + 54y - z = 0$$

$$y - 3z/2 + 10 = 0$$


Concepts

Kirchhoff's laws

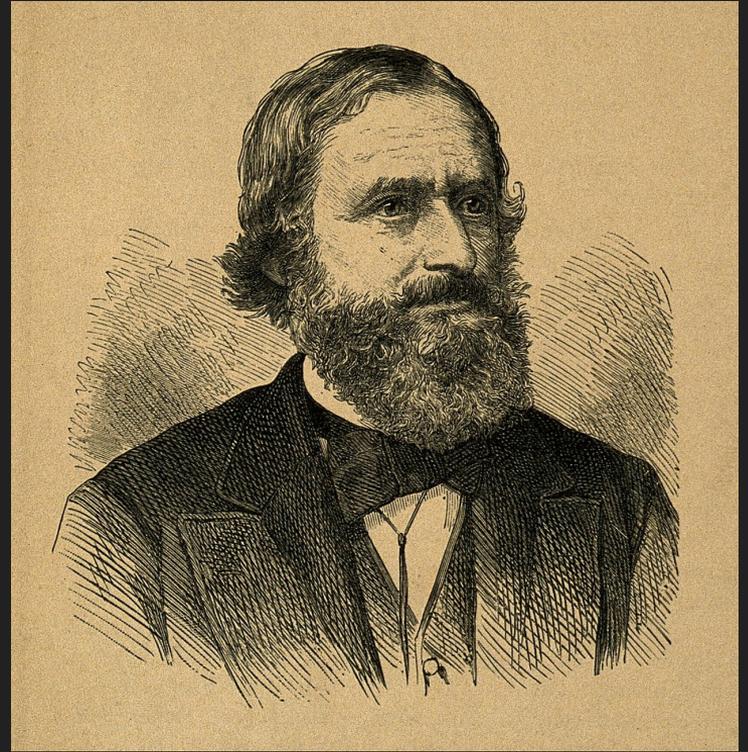- Current Law: The directed sum of currents in a line junction is zero.
- Voltage Law: The directed sum of voltages around a closed loop is zero.
- Postulated by Gustav Kirchhoff
- Allows us to calculate all currents and voltages in any circuit



Kirchhoff - Problem introduction

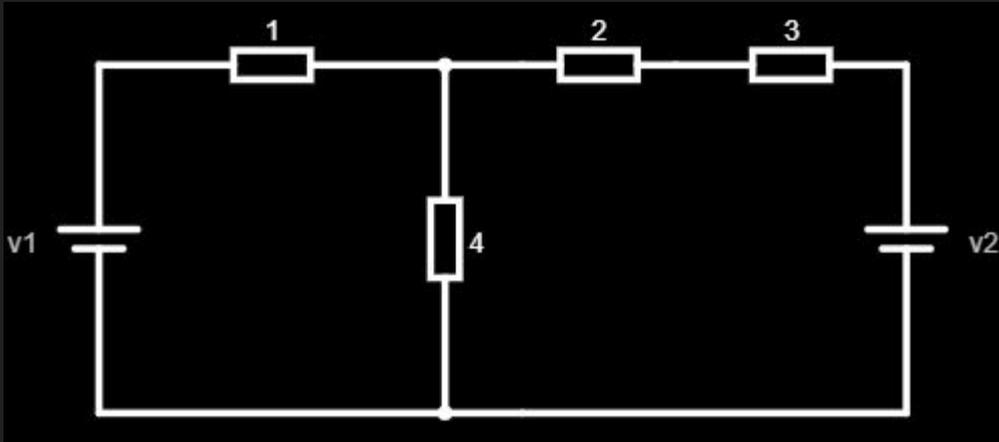

$V_1: 16V$

$R_1: 4\Omega$

$R_3: 2\Omega$


$V_2: 8V$

$R_2: 2\Omega$

$R_4: 8\Omega$

- Given this circuit, we want to know the current at R_2 .
- We could add R_2 and R_3 as they are in series, but what do we do with R_4 ? And what do we do with the multiple batteries?
- To solve this, we need to use Kirchhoff's laws.

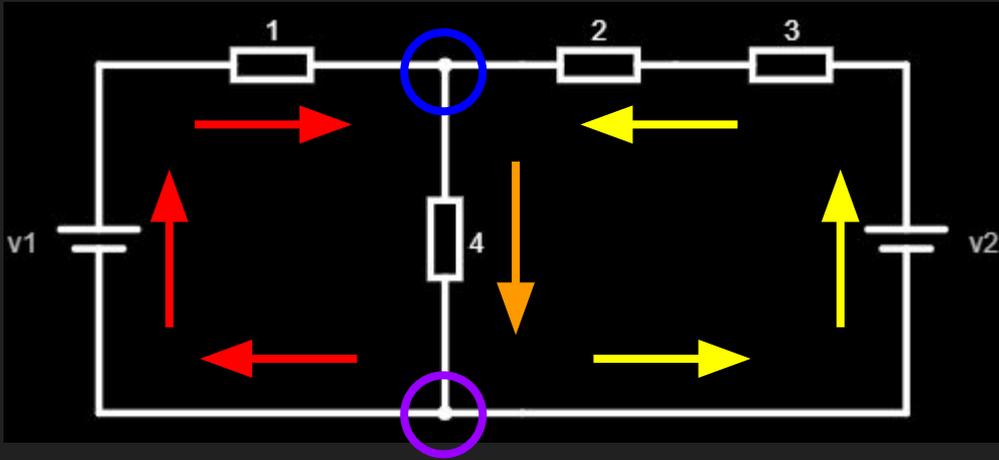Kirchhoff - Identify junctions and currents



$V_1: 16V$

$R_1: 4\Omega$

$R_3: 2\Omega$


$V_2: 8V$

$R_2: 2\Omega$

$R_4: 8\Omega$

- We identify junctions of the circuit, we will call them **J1** and **J2**
- We identify the currents and we decide their direction. We will call them **I_1** , **I_2** and **I_3** . Notice they go from junction to junction.

Kirchhoff - Get Junction equations

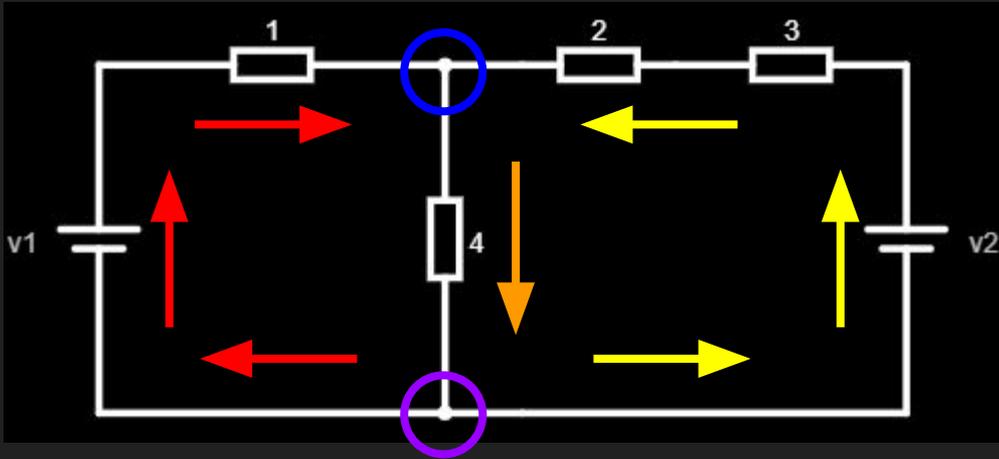

$V_1: 16V$

$R_1: 4\Omega$

$R_3: 2\Omega$

$V_2: 8V$

$R_2: 2\Omega$


$R_4: 8\Omega$

- Using the current law, we know that currents entering a junction minus currents leaving it equal 0.
- We get these equations:

$$J1: I_1 + I_3 - I_2 = 0$$

$$J2: I_2 - I_1 - I_3 = 0$$

Kirchhoff - Identify loops

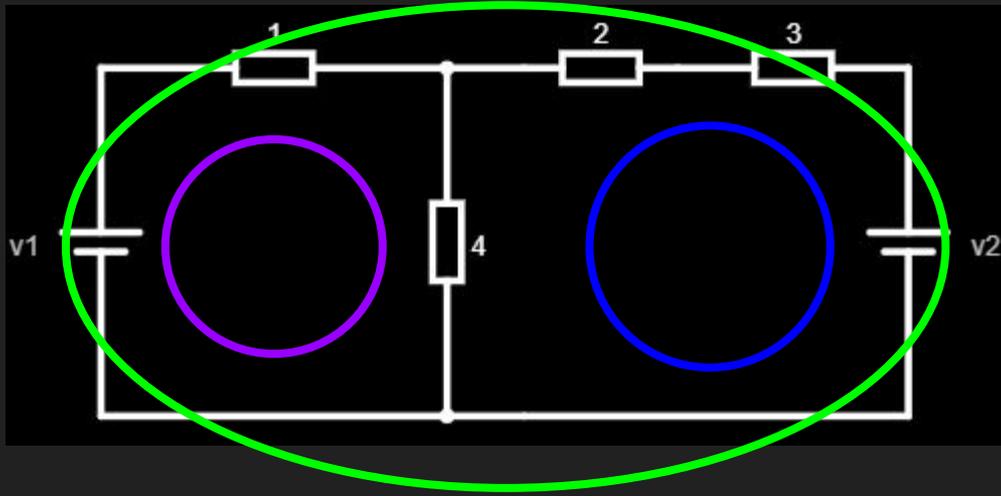

V1: 16V

R1: 4Ω

R3: 2Ω

V2: 8V

R2: 2Ω


R4: 8Ω

- We identify closed loops of the circuit, we will call them **L1**, **L2** and **L3**.
- We will decide that all loops flow clockwise.

Kirchhoff - Get loop equations - 1

- Using the loop law, we know that the sum of directed voltages in a loop is equal to 0.
- Batteries that go in the loop direction have a positive voltage
- Batteries that go against the loop direction have a negative voltage
- By Ohm's law we know a resistor has a voltage equal to $I * R$.
- Resistors whose current goes in the loop direction have a negative voltage
- Resistors whose current goes against the loop direction have a positive voltage

Kirchhoff - Get loop equations - 2

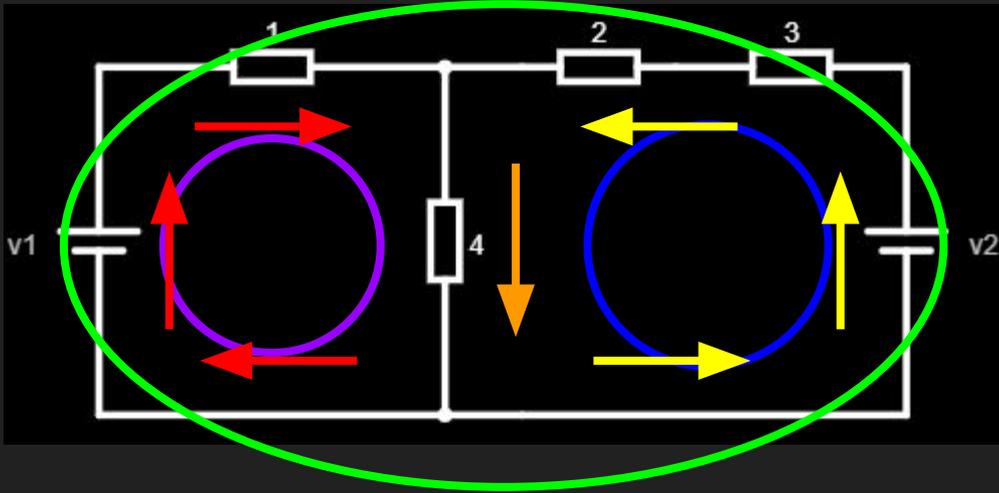

- We get these equations:

$$L1: +16 -4I1 -8I2 = 0$$

$$L2: +8I2 +2I3 +2I3 -8 = 0$$

$$L3: +16 -4I1 +2I3 +2I3 -8 = 0$$

V1: 16V

R1: 4Ω

R3: 2Ω

V2: 8V

R2: 2Ω

R4: 8Ω

Kirchhoff - Solve the system of equations - 1

- We have a system of 5 equations and 3 variables:

$$J1: I_1 + I_3 - I_2 = 0$$

$$J2: I_2 - I_1 - I_3 = 0$$

$$L1: +16 - 4I_1 - 8I_2 = 0$$

$$L2: +8I_2 + 2I_3 + 2I_3 - 8 = 0$$

$$L3: +16 - 4I_1 + 2I_3 + 2I_3 - 8 = 0$$

- We are going to solve it by substitution using 3 of these equations. There are many possible ways to solve it, try to pick the one you think will be easier.

Kirchhoff - Solve the system of equations - 2

- We will start solving L1 for I_1

$$+16 - 4I_1 - 8I_2 = 0$$

$$-4I_1 = +8I_2 - 16$$

$$4I_1 = -8I_2 + 16$$

$$I_1 = (+16 - 8I_2)/4$$

$$I_1 = +4 - 2I_2$$

Kirchhoff - Solve the system of equations - 3

- Then we will solve J1 for **I3**, replacing **I1** by the expression we got in previous step (**I1** = +4 -2**I2**)

$$+I1 +I3 -I2 = 0$$

$$+4 -2I2 +I3 -I2 = 0$$

$$+4 -3I2 +I3 = 0$$

$$I3 = +3I2 -4$$

Kirchhoff - Solve the system of equations - 4

- Finally we will solve L2 for I_2 , replacing I_3 by the expression we got in previous step ($I_3 = +3I_2 - 4$)

$$+8I_2 + 2I_3 + 2I_3 - 8 = 0$$

$$+20I_2 - 24 = 0$$

$$+8I_2 + 4I_3 - 8 = 0$$

$$I_2 = 24/20$$

$$+8I_2 + 4(+3I_2 - 4) - 8 = 0$$

$$I_2 = 1.2$$

$$+8I_2 + 12I_2 - 16 - 8 = 0$$

Kirchhoff - Solve the system of equations - 5

- Now that we know the value for **I2** (1.2) we just need to use the expressions for **I1** and **I3**

$$I_3 = +3I_2 - 4$$

$$I_1 = +4 - 2I_2$$

$$I_3 = +3*1.2 - 4$$


$$I_1 = +4 - 2*1.2$$

$$I_3 = -0.4$$

$$I_1 = 1.6$$

- Notice **I3** is negative, this means we got the wrong direction.

Kirchhoff - Solved!

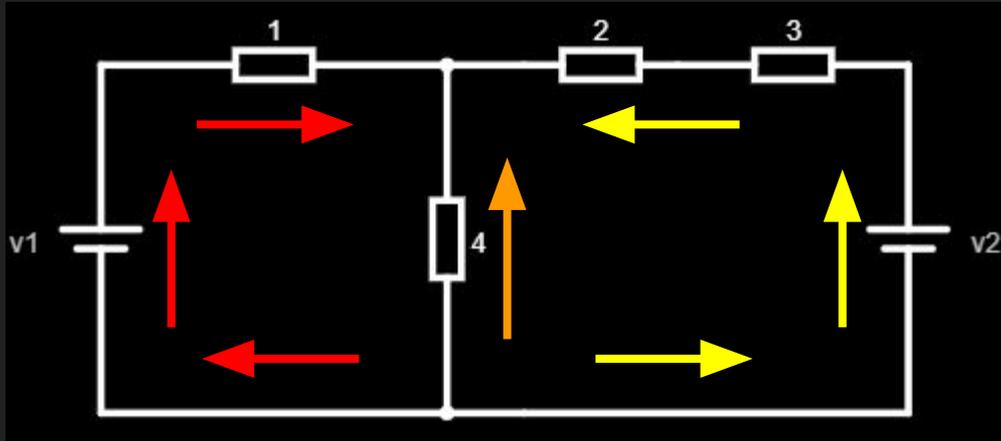

$V_1: 16V$

$V_2: 8V$

$R_1: 4\Omega$

$R_3: 2\Omega$

$R_2: 2\Omega$

$R_4: 8\Omega$

$I_1: 1.6A$

$I_2: 1.2A$

$I_3: 0.4A$



SCHOOL OF THE WEST

End of first module

Next module: DC electronics advanced